

2025 《计算机系统 I》课程小测 1

姓名： _____ 学号： _____ 判卷人： _____ 分数： _____/50

1、 Calculate the gate input cost for the **original** F and simplify it. (8 pts)

$$F = A(B + \bar{C}) + \bar{A}(\bar{B} + C) + BCD + \bar{B}\bar{C}D$$

- 2、 (12%) For the following Boolean functions F together with the don't-care conditions d, first draw a K-map, then obtain an optimized SOP and POS expression, separately.

$$F(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 5)$$

- a) (4%) Draw the K - map.
- b) (4%) List all the prime implicants and the essential prime implicants;
- c) (2%) Obtain the SOP optimization.
- d) (2%) Obtain the POS optimization.

- 3、采用一个 4 位全加器设计一个 4 位递增/递减器。当输入 $S = 0$ 时，电路是一个递增器；当 $S = 1$ 时，电路是一个递减器。（10 分）

- 4、(20%) 设计一个可控计数器。当控制输入 $C = 1$ 时，计数顺序为 $000 \rightarrow 100 \rightarrow 110 \rightarrow 111 \rightarrow 011 \rightarrow 000$ ；当 $C = 0$ 时，计数顺序为 $000 \rightarrow 100 \rightarrow 110 \rightarrow 010 \rightarrow 011 \rightarrow 000$ 。请写出状态表，状态方程和输出方程，并画出电路图。